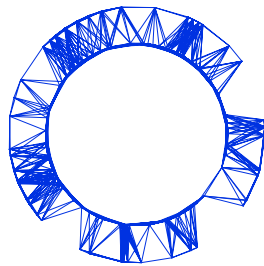


IPhO 2018  
Lisbon, Portugal



## Detailed Marking Scheme Experimental Problem 1

### Paper transistor

(Elvira Fortunato, Luís Pereira, Rui Igreja, Paul Grey, Inês Cunha, Diana Gaspar, Rodrigo Martins)

July 24, 2018

v1.4

Confidential

## Paper transistor (10 points)

### Part A. Circuit dimensioning (2.5 points)

#### A.1

|                           |     |
|---------------------------|-----|
| Apply Ohm's Law           | 0.1 |
| Obtain the output voltage | 0.1 |
| Total                     | 0.2 |

#### A.2

|  |     |
|--|-----|
| Five or more measurement for each resistance | 0.3 |
| Calculate the average                        | 0.1 |
| Uncertainty                                  | 0.1 |
| Total  | 0.5 |

[not reasonable enough number of points,  $-0.2\text{pt}$ ]

[Wrong or missing units  $-0.05\text{pt}$ ]

[Wrong resistance values  $-0.3\text{pt}$ ]

#### A.3

|                               |     |
|-------------------------------|-----|
| Expression for the resistance | 0.1 |
| Obtain $R_{\square}$          | 0.2 |
| Total                         | 0.3 |

#### A.4

|   |     |
|---|-----|
| Calculate the weighted average sheet resistance | 0.2 |
| Obtain the resistivity                          | 0.2 |
| Total   | 0.4 |

[missing the uncertainty,  $-0.1\text{pt}$ ]

[Wrong or missing units  $-0.05\text{pt}$ ]

## A.5

|   |     |
|---|-----|
| Expression for the theoretical $\kappa$       | 0.2 |
| Measurement of the resistances                | 0.1 |
| Experimental value of $\kappa$ and comparison | 0.2 |
| Total   | 0.5 |

## A.6

|  |     |
|--|-----|
| Measurement of the resistances $R_x$ and $R_y$ | 0.3 |
| Total  | 0.3 |

[*wrong or missing units in the table*,  $-0.05\text{pt}$ ; mixing up  $R_x$  and  $R_y$ ,  $-0.1\text{pt}$ ]

## A.7

|                                     |     |
|-------------------------------------|-----|
| Measurement of all $V_{out}$ values | 0.3 |
| Total                               | 0.3 |

[missing or wrong unit,  $-0.05\text{pt}$ ; wrong sign of  $V_{out}$ ,  $-0.1\text{pt}$ ]

## Part B. Characteristic Curves of the JFET transistor (4.5 points)

### B.1

|                                       |     |
|---------------------------------------|-----|
| Value within 20% of the correct value | 0.2 |
| Total                                 | 0.2 |

[missing or wrong unit  $-0.05\text{pt}$ ; missing *or wrong* uncertainty  $-0.05\text{pt}$ ]

### B.2

|  |     |
|--|-----|
| Measurements of $I_{DS}$ (first part)  | 0.3 |
| Measurements of $I_{DS}$ (second part, at least four sets of measurements for $V_{GS} < 0$ ) | 0.4 |
| Five or more sets of measurements for $V_{GS} < 0$   | 0.1 |
| Total  | 0.8 |

[wrong or missing current units,  $-0.1\text{pt}$ ; wrong number of significant digits in table entries,  $-0.05\text{pt}$ ]

## B.3

|                    |     |
|--------------------|-----|
| Expression for $f$ | 0.2 |
| Total              | 0.2 |

## B.4

|  |     |
|--|-----|
| Realize that $R_L = R_{DS} + \text{internal resistance of multimeter}$ | 0.2 |
| Calculation of $R_{DS}$ from nominal data                              | 0.3 |
| Apply correction factor $f$  | 0.5 |
| Subtract the voltage drop inside the multimeter                        | 0.2 |
| Total  | 1.2 |

## B.5

|  |     |
|--|-----|
| Plot, at least, five curves (0.1pt each) | 0.5 |
| Total                                    | 0.5 |

[use uncorrected  $V_{DS}$ ,  $-0.1$  pt; wrong or missing axes labels,  $-0.1$ pt]

## B.6

|  |     |
|--|-----|
| Obtain the experimental values from slopes | 0.3 |
| Plot the graph                             | 0.2 |
| Total                                      | 0.5 |

[any reasonable graph is worth 0.2; no graph analysis required]

## B.7

|                  |     |
|------------------|-----|
| Draw a good plot | 0.3 |
| Total            | 0.3 |

[wrong or missing magnitudes in axes labels,  $-0.05$ pt; wrong or missing units in axes labels,  $-0.05$ pt; plot the curve for a wrong  $V_{DS}$ ,  $-0.3$ pt; graph showing unreasonable deviation with respect to the transistor data,  $-0.2$ pt]

## B.8

|   |     |
|---|-----|
| Current $I_{DSS}$   | 0.1 |
| Obtain $V_p$ using the appropriate graphical method (plotting $\sqrt{I_{DS}}$ as a function of $V_{GS}$ ) | 0.2 |
| Comparison  | 0.1 |
| Total   | 0.4 |

[if  $V_p$  is not obtained from an appropriate graphical method, using a plot with linearized data, -0.05pt]

## B.9

|   |     |
|---|-----|
| Plot the transconductance curve                       | 0.1 |
| Obtain $g$ from the slope of the tangent to the curve | 0.2 |
| Comparison with model equation (2)                    | 0.1 |
| Total   | 0.4 |

## Part C: The Paper Thin Film Transistor (2.0 points)

### C.1

|   |     |
|---|-----|
| At least fifteen data points presented in the table | 0.8 |
| Total   | 0.8 |

[not using the appropriate multimeter range (2000  $\mu\text{A}$ ), -0.1pt; missing units, -0.1pt; data deviating too much from the expected behaviour, -0.2pt; IDS for the closed transistor is not the 1st value, -0.1pt; not enough points in the fast changing regime, -0.1pt]

### C.2

|  |     |
|--|-----|
| Draw a good plot   | 0.3 |
| Show the similarity <i>with a superposition of two exponential processes</i> | 0.1 |
| Subtraction of the long-time constant component                              | 0.4 |
| Determine $\tau_1$   | 0.4 |
| Total  | 1.2 |

[missing or wrong units in the plot -0.1pt]

## Part D. Inverter Circuit (1.0 points)

## D.1

|   |     |
|---|-----|
| Measurement of $R_L$ in the correct range                       | 0.1 |
| Measurement of, at least, eight points                          | 0.2 |
| Data showing a clear cut-off ( $V_{out}$ should go below 0.1 V) | 0.2 |
| Total   | 0.5 |

[missing units and/or wrong labels,  $-0.05\text{pt}$  each;  $\tau_1$  not used as time in between measurements,  $-0.1\text{pt}$ ]

## D.2

|  |     |
|--|-----|
| Draw a good plot, including the smooth trend curve | 0.5 |
| Total  | 0.5 |

[missing units and/or wrong labels,  $-0.05\text{pt}$  each; non-smooth curve (e.g. trend curve with spikes),  $-0.2\text{pt}$ ]